
NAME _____ CLASS _____

READING CIRCUIT DIAGRAMS

Use the symbol chart on Worksheet 6 or in your course notes to help you.


Each circuit below is powered by a battery at the bottom.

CIRCUIT 1

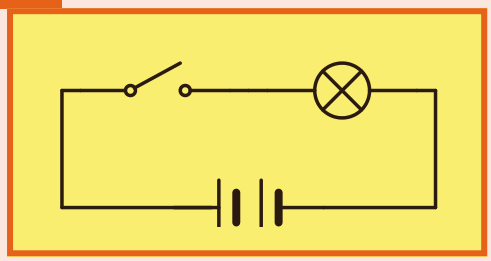


Name every component in this circuit and say what it does when the switch is closed.

CIRCUIT 2

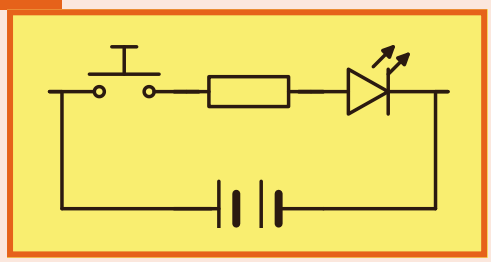

Name every component in this circuit and say what it does when the switch is closed.

CIRCUIT 3

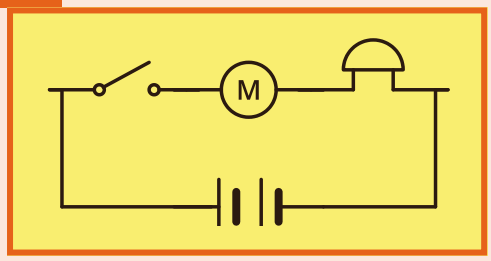

Name every component in this circuit and say what it does when the switch is closed.

4 Draw a circuit diagram for this description: *"A battery, a switch and two lamps all in one loop."* 4 marks